

Analog CMOS Integrated Circuit Design Cheat Sheet

By Xiao Ma (mxlol233@outlook.com)[<https://github.com/TuringKi/Analog-CMOS-Integrated-Circuit-Design-Cheat-Sheet>]

Model of MOS Transistors

Process parameters (n, V_{TH}, KP, V_E):

$$t_{OX} = \frac{L_{min}}{50} \quad (1)$$

$$t_{si} = \sqrt{\frac{2\epsilon_{si}(\Phi - V_{BD})}{qN_B}} \quad (2)$$

$$C_{OX} = \frac{\epsilon_{OX}}{t_{OX}} \quad (3)$$

$$C_D = \frac{\epsilon_{si}}{t_{si}} \quad (4)$$

$$KP = \mu C_{OX} \quad (5)$$

$$\beta = KP \frac{W}{L} \quad (6)$$

$$Q_{dep} = \sqrt{4q\epsilon_{si}|\Phi_F|N_{sub}} \quad (7)$$

$$V_{TH0} = \Phi_{MS} + 2\Phi_F + \frac{Q_{dep}}{C_{OX}} \quad (8)$$

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\Phi_F| + V_{BS}} - \sqrt{|2\Phi_F|}) \quad (9)$$

$$n = \frac{\gamma}{\sqrt{|2\Phi_F| + V_{BS}}} = 1 + \frac{C_D}{C_{OX}} \quad (10)$$

In linear region:

$$I_{DS} = \beta[(V_{GS} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2] \quad (11)$$

$$R_{on} = \frac{1}{\beta(V_{GS} - V_{TH})} \quad (12)$$

Channel-Length modulation in saturation region:

$$K' = \frac{KP}{2n} \quad (13)$$

$$\lambda = \frac{1}{V_E L} \quad (14)$$

$$I_{DS} = K' \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (15)$$

$$r_o = \frac{\partial V_{DS}}{\partial I_{DS}} \approx \frac{1}{\lambda I_{DS}} = \frac{V_E L}{I_{DS}} \quad (16)$$

Saturation region has three distinctive regions: weak-inversion (exponential region), strong-inversion, and velocity saturation.

Value Examples In 0.35μm Process Nodes

Names	Symbols	Values
dielectric constant of sub-silicon	ϵ_{si}	1 pF/cm
dielectric constant of gate-oxide	ϵ_{OX}	0.34 pF/cm
electron charge	q	1.6×10^{-19} C
minium channel length	L_{min}	0.35 μm
width of gate-oxide	t_{OX}	0.1 nm
width of depletion layer	t_{si}	7 nm
junction built-in voltage	Φ	0.6 V
drain-bulk voltage	V_{BD}	-3.3V
gate-oxide capacitance	C_{OX}	0.5 μF/cm ²
depletion layer capacitance	C_D	0.1 μF/cm ²
bulk doping level	N_B	4×10^{17} cm ⁻³
P type mobility rate	μ_p	250 cm ² /Vs
N type mobility rate	μ_n	600 cm ² /Vs
N type KP	KP_n	300 μA/V ²
	n	1.2...1.5
	$ 2\Phi_F $	0.6 V
	γ	0.5...0.8 V ^{1/2}
N type K'	K'_n	100 μA/V ²
P type K'	K'_p	40 μA/V ²
	V_{GSTt}	70 mV
	v_{sat}	10 ⁷ cm/s
	θL	0.2 μm/V

Weak-Inversion

$$I_{DS} = I_{D0} \frac{W}{L} e^{\frac{V_{GS}}{n \frac{KT}{q}}} \quad (17)$$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \frac{I_{DS}}{n \frac{KT}{q}} \quad (18)$$

strong-inversion

Ignore channel-length modulation:

$$I_{DS} = K' \frac{W}{L} (V_{GS} - V_{TH})^2 \quad (19)$$

$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TH}} \quad (20)$$

Transition Point Between Weak-Inversion and Strong-Inversion

The voltage and current at transition point between weak-inversion and strong-inversion:

$$V_{GSt} = 2n \frac{KT}{q} + V_{TH} \quad (21)$$

$$I_{DS t} \approx K' \frac{W}{L} (2n \frac{KT}{q})^2 \quad (22)$$

EKV model, a smooth model for weak-inversion and strong-inversion regions:

$$I_{DS} = K' \frac{W}{L} (V_{GS} - V_{TH})^2 [\ln(1 + e^{\frac{V_{GS}}{V_{GSt}}})]^2 \quad (23)$$

Let:

$$v = \frac{V_{GS}}{V_{GSt}} \quad (24)$$

$$i = \frac{I_{DS}}{I_{DS t}} = [\ln(1 + e^v)]^2 \quad (25)$$

then,

$$v = \ln(e^{\sqrt{i}} - 1) \quad (26)$$

$$V_{GS} - V_{TH} = V_{GSTt} \ln(e^{\sqrt{i}} - 1) \quad (27)$$

where:

$$V_{GSTt} = V_{GSt} - V_{TH} = 2n \frac{KT}{q} \quad (28)$$

When $v = 1$, $i = 1$, we also have:

$$I_{DS t} = K' \frac{W}{L} (V_{GSt} - V_{TH})^2 \quad (29)$$

Velocity Saturation

$$I_{DS} = WC_{OX} v_{sat} (V_{GS} - V_{TH}) \quad (30)$$

$$g_m = WC_{OX} v_{sat} \quad (31)$$

Transition Point Between Strong-Inversion and Velocity Saturation

A smooth model for strong-inversion and velocity saturation regions:

$$I_{DS} = \frac{K' \frac{W}{L} (V_{GS} - V_{TH})^2}{1 + \theta(V_{GS} - V_{TH})} \quad (32)$$

where:

$$\theta = \frac{\mu}{2n v_{sat} L} \quad (33)$$

θL is constant:

$$\theta L = \frac{\mu}{2n v_{sat}} \quad (34)$$

$$g_{m, sat} = WC_{OX} v_{sat} = \frac{K' W}{\theta L} \quad (35)$$

The voltage and current at transition point between strong-inversion and velocity saturation:

$$V_{GSt} = \frac{1}{\theta} + V_{TH} = 2nL \frac{v_{sat}}{\mu} + V_{TH} \quad (36)$$

$$I_{DS t} = K' W L (2n \frac{v_{sat}}{\mu})^2 \quad (37)$$

1st Order Time-constants and Transfer-Constants (TTCs)

A system with N frequency-dependent elements, th transfer function in complex-frequency form:

$$H_s = \frac{a_0 + a_1 s}{1 + b_1 s} \quad (38)$$

where:

$$a_0 = H^0 \quad (39)$$

$$b_1 = \sum_{i=1}^N \tau_i^0 \quad (40)$$

$$a_1 = \sum_{i=1}^N \tau_i^0 H^i \quad (41)$$

where H^0 is the low-frequency gain:

$$H^0 : C_1, C_2, \dots, C_N = 0 \quad (42)$$

or:

$$H^0 : L_1, L_2, \dots, L_N = 0 \quad (43)$$

For capacitor:

$$\tau_i^0 = C_i R_i^0 \quad (44)$$

or for inductor:

$$\tau_i^0 = \frac{L_i}{R_i^0} \quad (45)$$

where R_i^0 is the resistance seen by the capacitor C_i looking into port i with all other reactive elements connected to the other ports at their zero value (hence the superscript), namely open-circuited capacitors (and short circuited inductors):

$$R_i^0 : C_1, C_2, C_{i-1}, C_{i+1}, \dots, C_N = 0 \quad (46)$$

or:

$$R_i^0 : L_1, L_2, \dots, L_{i-1}, L_{i+1}, \dots, L_N = 0 \quad (47)$$

Bandwidth estimation by 1st-order TTCs:

$$\omega_h \approx \frac{1}{b_1 - \frac{a_1}{a_0}} = \frac{1}{\sum_{i=1}^N \tau_i^0 (1 - \frac{H^i}{H^0})} \quad (48)$$

2nd Order Time-constants and Transfer-Constants (TTCs)

A system with 2 frequency-dependent elements, th transfer function:

$$H_s = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2} \quad (49)$$

where:

$$a_0 = H^0 \quad (50)$$

$$b_1 = \tau_1^0 + \tau_2^0 \quad (51)$$

$$a_1 = \tau_1^0 H^1 + \tau_2^0 H^2 \quad (52)$$

$$b_2 = \tau_1^0 \tau_2^1 = \tau_2^0 \tau_1^2 \quad (53)$$

$$a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12} \quad (54)$$

in which, H^1 (H^2) evaluated with the frequency-dependent element at the port 1(2) at its infinite value (i.e., shorted capacitors and open inductors):

$$H^1 : C_1 = \infty, C_2 = 0 \quad (55)$$

$$H^2 : C_1 = 0, C_2 = \infty \quad (56)$$

or:

$$H^1 : L_1 = \infty, L_2 = 0 \quad (57)$$

$$H^2 : L_1 = 0, L_2 = \infty \quad (58)$$

For capacitor:

$$\tau_1^0 = C_1 R_1^0 \quad (59)$$

$$\tau_2^0 = C_2 R_2^0 \quad (60)$$

$$\tau_1^2 = C_1 R_1^2 \quad (61)$$

$$\tau_2^1 = C_2 R_2^1 \quad (62)$$

or for inductor:

$$\tau_1^0 = \frac{L_1}{R_1^0} \quad (63)$$

$$\tau_2^0 = \frac{L_2}{R_2^0} \quad (64)$$

$$\tau_1^2 = \frac{L_1}{R_1^2} \quad (65)$$

$$\tau_2^1 = \frac{L_2}{R_2^1} \quad (66)$$

in which, R_1^2 is the resistance seen by C_1 (the subscript) when C_2 (the superscript) is infinite valued (shorted):

$$R_1^2 : C_2 = \infty \quad (67)$$

$$R_2^1 : C_1 = \infty \quad (68)$$

or:

$$R_1^2 : L_2 = \infty \quad (69)$$

$$R_2^1 : L_1 = \infty \quad (70)$$

General Time-constants and Transfer-Constants (TTCs)

A system with N frequency-dependent elements, th transfer function:

$$H_s = \frac{a_0 + a_1 s + a_2 s^2 \dots + a_n s^n + \dots}{1 + b_1 s + b_2 s^2 \dots + b_n s^n + \dots} \quad (71)$$

where:

$$a_0 = H^0 \quad (72)$$

$$b_1 = \sum_{i=1}^N \tau_i^0 \quad (73)$$

$$a_1 = \sum_{i=1}^N \tau_i^0 H^i \quad (74)$$

$$b_2 = \sum_{i=1}^{i < j} \sum_{j=i+1}^{j \leq N} \tau_i^0 \tau_j^i \quad (75)$$

$$a_2 = \sum_{i=1}^{i < j} \sum_{j=i+1}^{j \leq N} \tau_i^0 \tau_j^i H^{ij} \quad (76)$$

$$b_n = \sum_{i=1}^{i < j} \sum_{j=i+1}^{j < k} \sum_{k=j+1}^{k < \dots \leq N} \tau_i^0 \tau_j^i \tau_k^{ij} \dots \quad (77)$$

$$a_n = \sum_{i=1}^{i < j} \sum_{j=i+1}^{j < k} \sum_{k=j+1}^{k < \dots \leq N} \tau_i^0 \tau_j^i \tau_k^{ij} \dots H^{ijk\dots} \quad (78)$$

and for capacitor:

$$\tau_i^0 = C_i R_i^0 \quad (79)$$

$$\tau_i^{jk\dots} = C_i R_i^{jk\dots} \quad (80)$$

or for inductor:

$$\tau_i^0 = \frac{L_i}{R_i^0} \quad (81)$$


$$\tau_i^{jk\dots} = \frac{L_i}{R_i^{jk\dots}} \quad (82)$$

In the form of zeros and poles:

$$H_s = a_0 \frac{(1 - \frac{s}{z_1})(1 - \frac{s}{z_2}) \dots (1 - \frac{s}{z_m})}{(1 - \frac{s}{p_1})(1 - \frac{s}{p_2}) \dots (1 - \frac{s}{p_n})} \quad (83)$$

Operational-Amp: Biasing Circuits

Common Source, with resistance R_D :

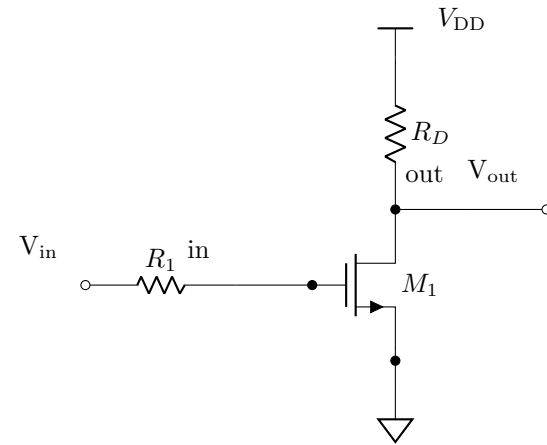


Transfer function of voltage gain in low-frequency:

$$A_v^0 = \frac{V_{out}}{V_{in}} = -g_m R_D \quad (84)$$

consider channel-length modulation:

$$A_v^0 = \frac{V_{out}}{V_{in}} = -g_m R_D || r_o = -g_m \frac{R_D r_o}{R_D + r_o} \quad (85)$$

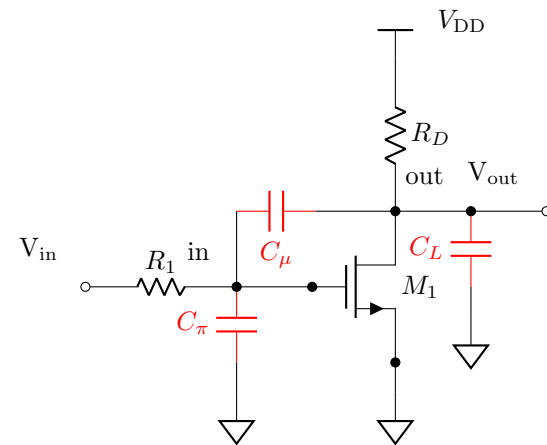Consider high-frequency gain with 3 capacitors c_π, c_μ, c_L :



$$\tau_\pi^0 = C_\pi (R_1 || R_D) \quad (86)$$

$$\tau_\mu^0 = C_\mu (R_{left} + R_{right} + G_m R_{left} R_{right}) = C_\mu (R_1 + R_D + g_m R_1 R_D) \quad (87)$$

$$\tau_L^0 = C_L R_D \quad (88)$$

$$\tau_\mu^\pi = C_\mu R_D \quad (89)$$